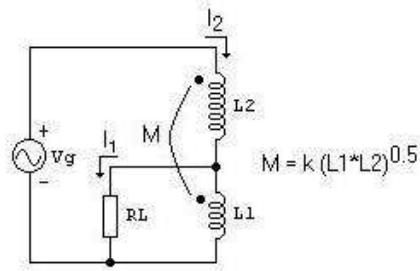


Useful Calculations for better understanding the use of The Bogen T-725 Autotransformer

Consider a lossless autotransformer driven by a voltage source V_g supplying power to a resistor R_L . See figure below.



Lossless autotransformer with
resistive load

Mesh equations describing the above network can be written as:

$$V_g = j\omega(L_2 + M)I_2 + j\omega(L_1 + M)(I_2 - I_1) \quad \dots(1)$$

$$I_1 = \frac{1}{R_L} [j\omega L_1(I_2 - I_1) + j\omega M I_2] \quad \dots(2)$$

From the above equation:

$$(R_L + j\omega L_1)I_1 = j\omega(L_1 + M)I_2$$

Then,

$$I_1 = \frac{j\omega(L_1 + M)}{R_L + j\omega L_1} I_2 \quad \dots(3)$$

Eq. (1) may be arranged as:

$$V_g = j\omega I_2(L_1 + L_2 + 2M) - j\omega I_1(L_1 + M)$$

Substituting eq. (3) into the above expression:

$$V_g = j\omega I_2(L_1 + L_2 + 2M) + \frac{\omega^2(L_1 + M)^2}{R_L + j\omega L_1} I_2$$

$$\begin{aligned}
&= \frac{j\omega I_2(L_1 + L_2 + 2M)R_L - \omega^2 L_1 I_2(L_1 + L_2 + 2M) + \omega^2(L_1 + M)^2 I_2}{R_L + j\omega L_1} \\
&= \frac{j\omega I_2(L_1 + L_2 + 2M)R_L + \omega^2 I_2(M^2 - L_1 L_2)}{R_L + j\omega L_1}
\end{aligned}$$


The mutual inductance M of L₁ and L₂ is given by $M = k(L_1 L_2)^{0.5}$, where k is the coupling coefficient. For values of k very close to unity, $M^2 - L_1 L_2$ nearly vanishes and :

$$V_g = \frac{j\omega I_2(L_1 + L_2 + 2M)R_L}{R_L + j\omega L_1}$$

The input admittance of the autotransformer network is computed as:

$$\begin{aligned}
\frac{I_2}{V_g} &= \frac{R_L + j\omega L_1}{j\omega(L_1 + L_2 + 2M)R_L} \\
&= \frac{1}{j\omega(L_1 + L_2 + 2M)} + \frac{L_1}{(L_1 + L_2 + 2M)R_L} \\
&= \frac{1}{j\omega(L_1 + L_2 + 2M)} + \frac{1}{\left(1 + \frac{L_2}{L_1} + \frac{2M}{L_1}\right)R_L}
\end{aligned}$$

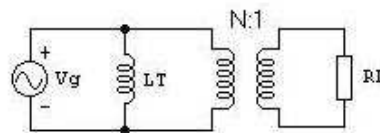which suggests the following transformer-like network equivalent:



$$L_T = L_1 + L_2 + 2M$$

$$M = (L_1 * L_2)^{0.5} \quad (k = 1)$$

$$\begin{aligned}
N^2 &= 1 + (L_2/L_1) + (2M/L_1) = L_T/L_1 \\
&= 1 + (L_2/L_1) + 2(L_2/L_1)^{0.5}
\end{aligned}$$


Transformer-like network equivalent of the autotransformer loaded by a resistive load RL.

$L_T = L_1 + L_2 + 2M$ is the measured inductance of the whole winding and L_1 is the inductance measured from the tap to the lower end of the winding.

Impedance transformation ratios are then $N^2 = L_T / L_1$ for each tap. The impedance ratio at 300 Hz or whatever frequency in the autotransformer's pass band is approximately equal (for $k \sim 1$) to the inductance ratio. Each tap is recognized by its impedance. I find it useful to calculate things at 300Hz and then scale the figures to the desired frequency. If it is desired 40k ohms to be the maximum impedance point, then it is a simple matter of calculating $40 * L_1 / L_T$ in kohms to find the corresponding impedance for the selected tap.

This is the methodology for determining the corresponding impedances assigned to each tap in the Bogen T-725 autotransformer (and for any other useful autotransformer for audio applications).



The Bogen T-725 Autotransformer

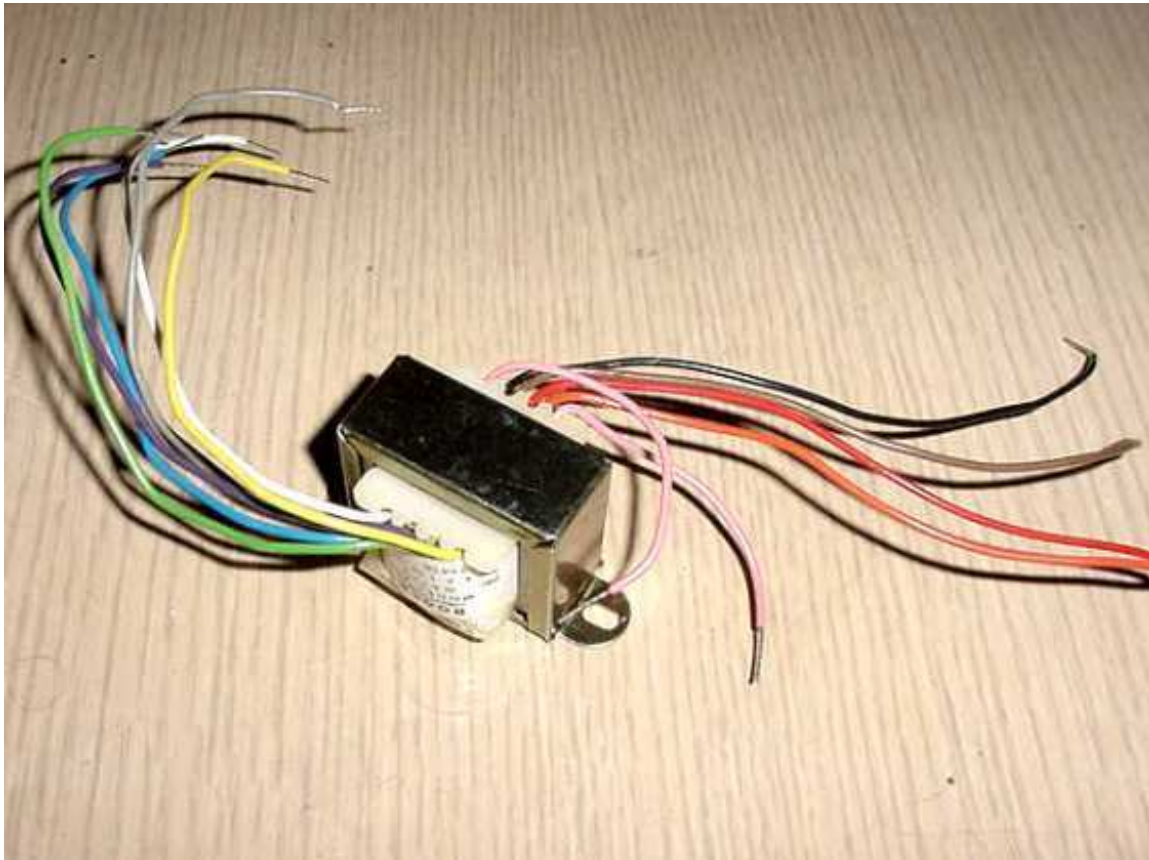

Bogen Specs.


All values are relative to the black (blk) tap.

| Color | Resistance | Inductance | XL @ 300 hz | Rounded Value |
|--------------|-------------|------------|--------------|---------------|
| White (WH) | 1424.3 ohms | 24 H | 45.239k ohms | 40k ohms |
| Gray (GRY) | 886.4 ohms | 12.04 H | 22.694k ohms | 20k ohms |
| Violet (VIO) | 516.5 ohms | 6.06 H | 11.423k ohms | 10k ohms |
| Blue (BLU) | 260.1 ohms | 3.04 H | 5.730k ohms | 5k ohms |
| Green (GRN) | 81.8 ohms | 1.565 H | 2.950k ohms | 2.5k ohms |
| Yellow (YEL) | 56 ohms | 787 mH | 1.483k ohms | 1.2k ohms |
| Orange (OR) | 38.2 ohms | 398 mH | 750.2 ohms | 600 ohms |
| Red (RED) | 26 ohms | 197 mH | 371.3 ohms | 300 ohms |
| Brown (BRN) | 18.2 ohms | 98 mH | 184.7 ohms | 150 ohms |
| Pink to Pink | 0.5 ohms | 5.23 mH | 9.86 ohms | 8 ohms |

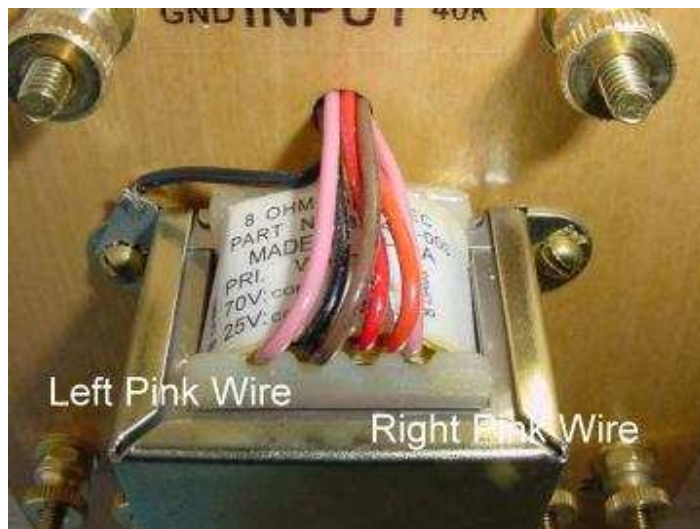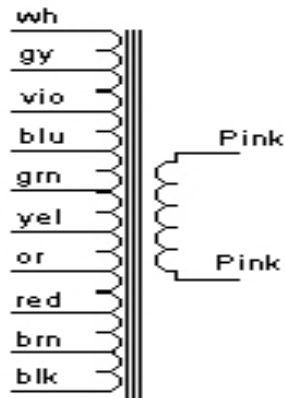

All values are relative to the left side pink tap.

| Color | Impedance @ 300Hz |
|----------|-------------------|
| White | 40k ohms |
| Gray | 20k ohms |
| Violet | 10k ohms |
| Blue | 5k ohms |
| Green | 2.5k ohms |
| Yellow | 1.5k ohms |
| Orange | 900 ohms |
| Red | 500 ohms |
| Brown | 250 ohms |
| Pink (R) | 8 ohms |

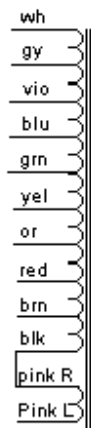

References

1. Schmarder, Dave “Uses for the Bogen T-725 Audio Transformer”
<http://www.schmarder.com/radios/misc-stuff/t-725.htm>
2. Schmarder, Dave “Simple Matching Circuit Using Bogen Transformer”
<http://www.schmarder.com/radios/misc-stuff/transformer.htm>
3. Bringhurst, Steve “S-T-M Calrad / Bogen ‘Select to Match’ Impedance Matching Circuit” <http://www.crystalradio.net/soundpowered/matching/index.shtml>

Ramon Vargas Patron
rvargas@inictel.gob.pe
Lima-Peru, South America
September 9th 2004