

$$U_{be} = 2 \cdot \cos(\omega t)$$


$$\omega = 10^6 \text{ rad/s}$$

$$U_{be} = 2 \cdot e^{j\omega t}$$


$$R_1 = 1k$$

$$R_2 = 1k$$

$$L = 2 \text{ mH}$$

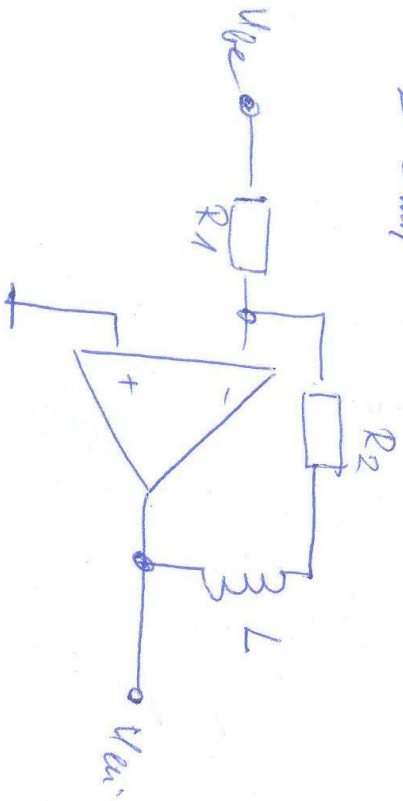

$\Rightarrow$

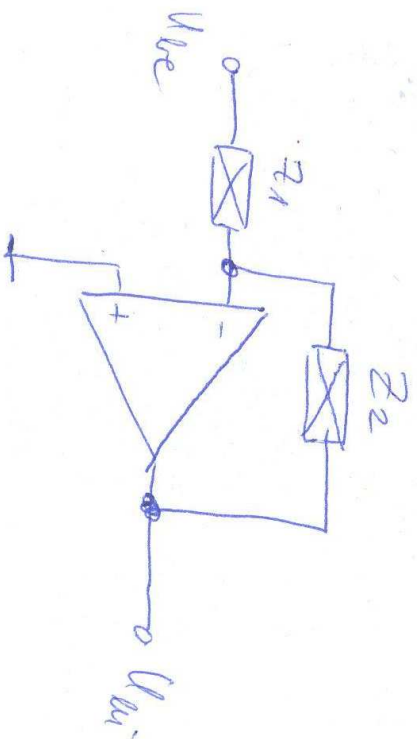



$$\frac{U_{wi}}{U_{be}} = - \frac{Z_2}{Z_1} = - \frac{R_2 + j\omega L}{R_1} = - \frac{R_2}{R_1} - j \frac{\omega L}{R_1} = -1 - j \frac{10^6 \cdot 2 \cdot 10^{-3}}{1000}$$

$$= -1 - j2 = \sqrt{5} \cdot e^{j243,44^\circ} = \sqrt{5} \cdot e^{-j116,56^\circ}$$

$$U_{wi} = U_{be} \cdot \sqrt{5} \cdot e^{-j116,56^\circ} = 2 \cdot e^{j\omega t} \cdot \sqrt{5} \cdot e^{-j116,56^\circ} =$$

$$= 2\sqrt{5} \cdot e^{j(\omega t - 116,56^\circ)} \text{ V} = 2\sqrt{5} \cdot \cos(\omega t - 116,56^\circ)$$

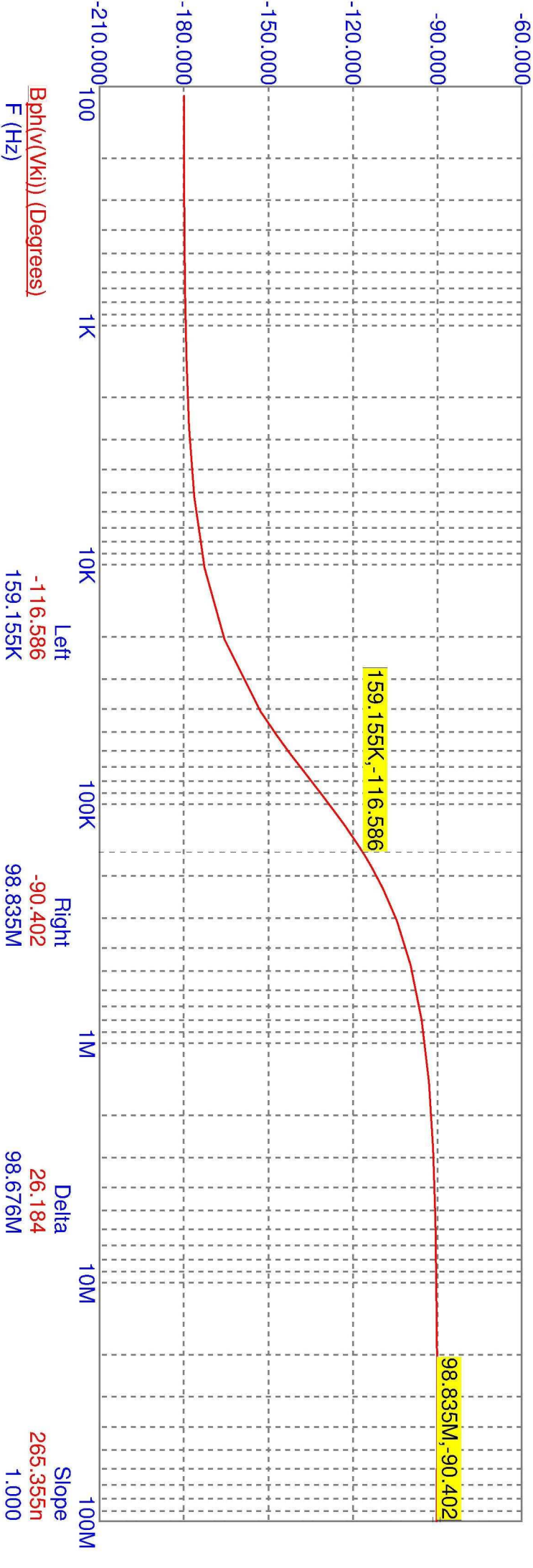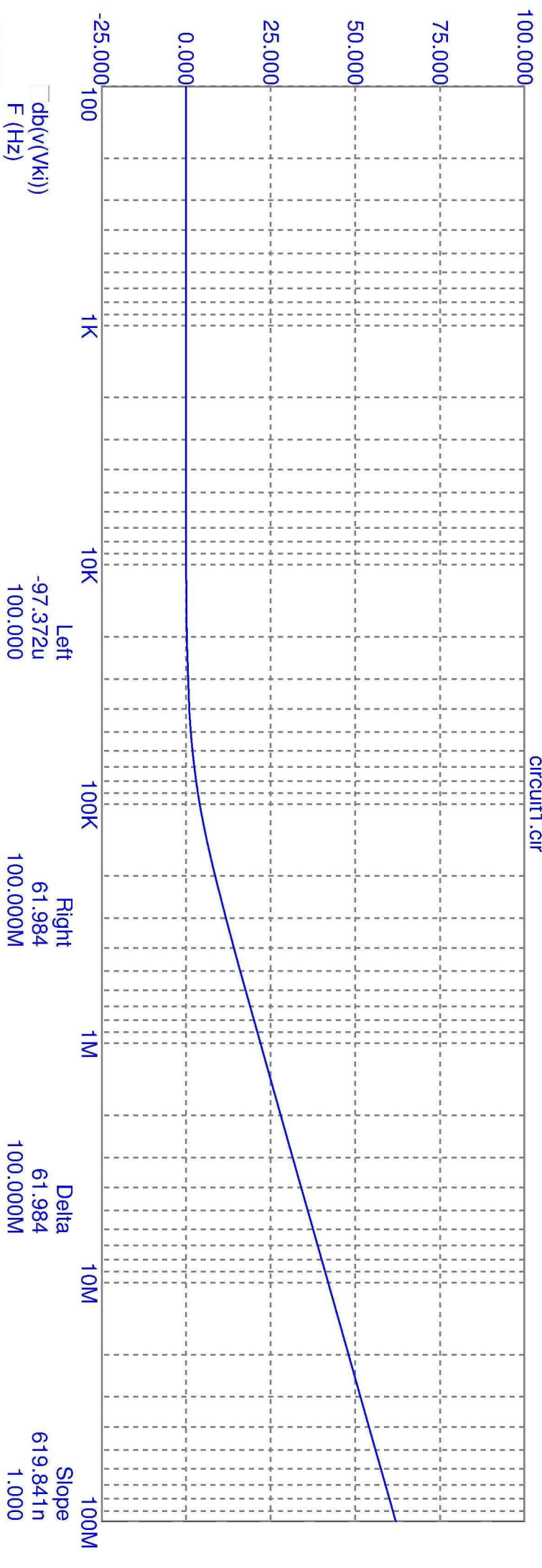Micro-Cap 9 Evaluation Version  
circuit1.cir



Micro-Cap 9 Evaluation Version  
circuit1.cir

