
Board Layout Recommendations

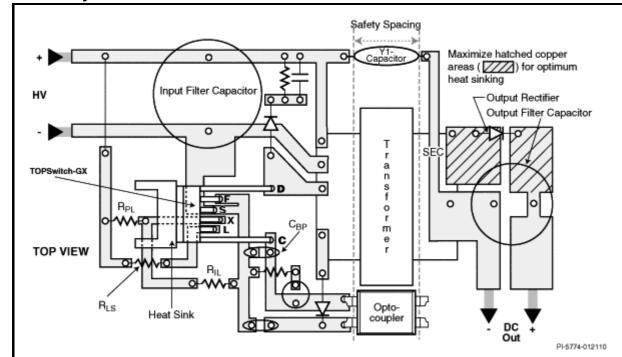



Click on the "Show me" icon to highlight relevant areas on the sample layout.

	Description	Show Me
1	Minimize loop area formed by drain, clamp and transformer	?
2	Bias winding and bias capacitor are a power connection and therefore returned to Kelvin connection at SOURCE pin	
3	Any traces to the L or X pins should be kept as short as possible and away from the DRAIN trace to prevent noise coupling	?
4	Place line sense resistors RLS1 and RLS2 as close to the L pin as possible	?
5	Minimize loop area formed by secondary winding, the output diode and the output filter capacitor	?

2014.01.17. 12:44:04