

This completely new amplifier circuit incorporates most of the features of our Ultra-LD Mk4 200W amplifier module but uses easy-to-solder through-hole components. There are no tiny surface mount components.

Over the last 15 years or so, SILICON CHIP has published a number of very popular audio amplifier modules. The first of these was the SC480, described in the January & February 2003 issues.

Best described as a work-horse, this amplifier was and still is very easy to assemble and get going, and countless thousands have been built. Indeed, you can still purchase kits for these modules from Altronics & Jaycar.

The next very popular amplifier module was the 20W Class-A module published in 2007. We billed this as “having the lowest distortion of any amplifier ever published... anywhere in the world!”

Very keen audiophiles have built it in large numbers but being Class-A, it does have the normal drawback of being quite inefficient and therefore it dissipates a lot of heat for its modest power output of 20 watts.

Finally, the next most notable amplifier module was the Ultra-LD Mk4 design which not only has high output power but its very low harmonic distortion levels challenge even those achieved by the 20W Class-A design. Indeed, the 110W version of the Ultra-LD effectively renders the modestly-powered 20W Class-A design irrelevant.

Why would you build that Class-A design when you can build a much more powerful Class-AB design for the same money and with virtually indistinguishable performance?

So why are we producing this new SC200 module? Firstly, we have felt that while the SC480 design has been very successful, its distortion and noise performance is pretty mediocre when compared to the latter two designs. In short, it is old-hat and well overdue for a major upgrade.

Second, while the Ultra-LD Mk.4 amplifier module is virtually state-of-the-art, it does have the drawback that it uses mainly surface-mount components and while many have been built, it would have been far more popular if it used through-hole components – ones that are much easier to solder!

So in designing the SC200 module, we have tried to make it much easier to build and at the same time, produce a module which is far ahead of the SC480 in all aspects of its performance. All the semiconductors on the PCB are con-

ventional through-hole components. Also the small-signal transistors are readily available types and while the input pair of transistors won't give quite the same extremely low noise performance of our previous Ultra-LD Mk.3 & Mk.4 designs, they are cheap and readily available.

The other major difference between the new SC200 design and the Ultra-LD Mk.4 is that it does not use the exotic five-lead On Semiconductor “ThermalTrak” NJ3281D/NJL1302D output transistors which have integral power diodes for quiescent current stabilisation. Instead, this new design uses conventional 3-lead power transistors from Fairchild, types FJA4313 and FJA4213.

While the ThermalTrak transistors are largely responsible for the excellent performance of the Ultra-LD amplifiers, they are rather expensive at \$8.90 each (current retail price) and that adds up if you're building a multi-channel amplifier.

And unfortunately, as our experience has shown, they never quite delivered on their promise to provide a stable quiescent current over the operating temperature range, without the need for adjustment.

We'll discuss the new output devices more later.

Main features

The main features of this new module, which we've called the SC200, indicative of its 200-watt power output into a 4-ohm load, are very similar to those of the Ultra-LD Mk.4. And while it will replace the work-horse SC480, we would like to think its performance will be very much in the thoroughbred class!

It certainly delivers more power than the SC480, for a similar price to build. Those main features are listed in a separate panel but some require additional comment.

Apart from exceptional performance, the SC200 has quite a few features which were not thought of when we produced the SC480. These include on-board LEDs which indicate if the power rails are present and which change colour if the DC fuses blow.

And there is the clipping indicator circuit which drives a LED to show when the amplifier is being over-driven. This LED can be mounted on the amplifier front panel if desired and can be wired to multiple modules to indicate when any channel is clipping. Or you can simply have a

Main features

- **Easy to build**
- **Uses low cost parts**
- **Low distortion and noise**
- **Compact PCB**
- **Able to produce specified power output on a continuous basis with passive cooling**
- **Onboard DC fuses**
- **Power indicator LEDs**
- **Fuse OK/blown indicator LEDs**
- **Clipping indicator LED**
- **Clean overload recovery with low ringing**
- **Clean square wave response with low ringing**
- **Tolerant of hum & EMI fields**
- **Survives brief short circuits & overload without blowing fuses**
- **Quiescent current adjustment with temperature compensation**
- **Output offset voltage adjustment**
- **Output protection diodes (for driving 100V line transformers and electrostatic speakers)**

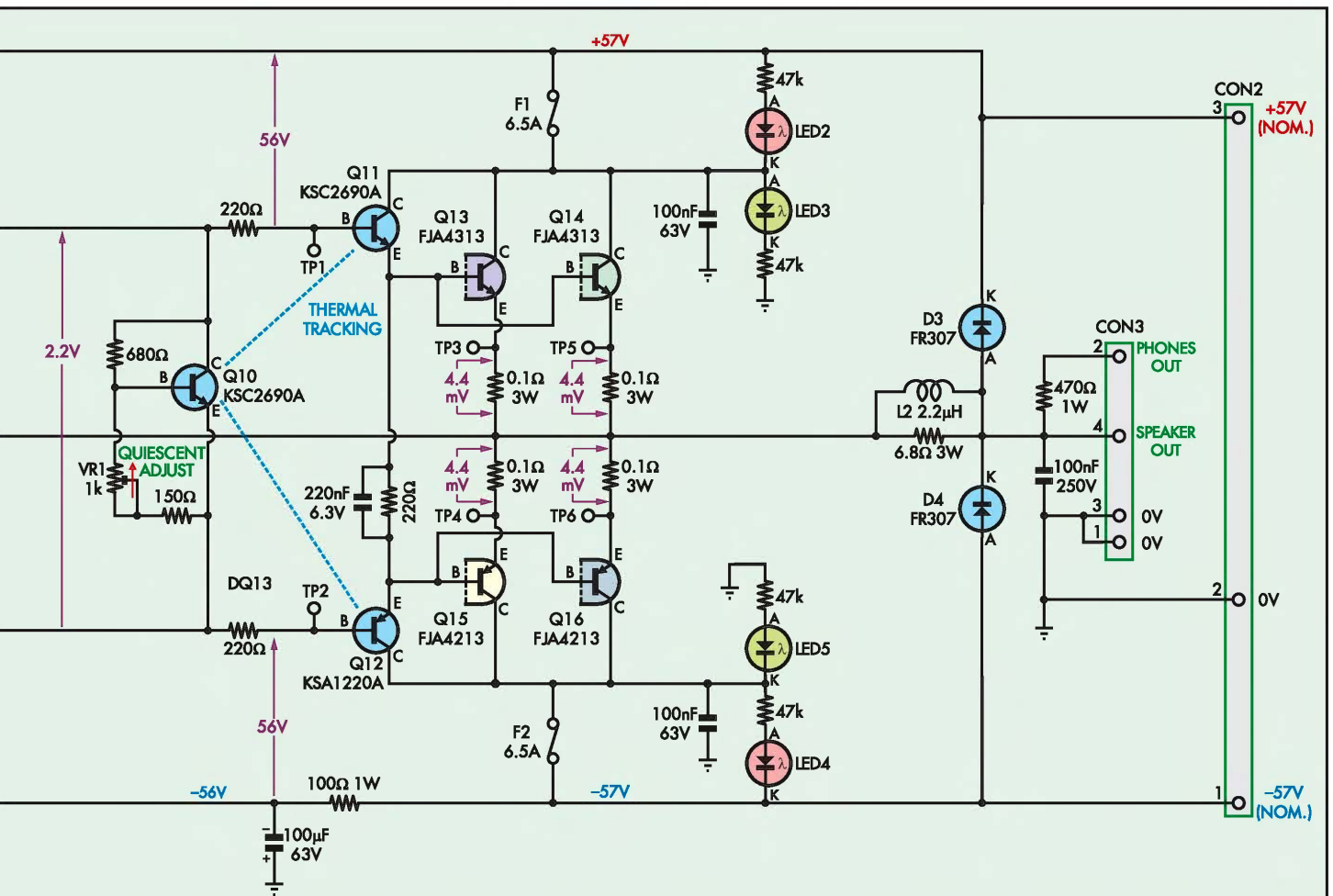


Fig.1: the complete circuit for the SC200 amplifier module minus the circuitry for the clipping detector, which is shown separately in Fig.2. Q1 and Q2 are the input transistors while Q5 and Q6 are the constant-current source. The signal from the collector of Q1 is fed to the base of Q7, which together with Q8 forms the voltage amplification stage. Q9 is the constant current load for Q8, providing very linear operation. Q10 is the V_{BE} multiplier and provides a floating voltage source which biases the complementary Darlington output stage.

sistor Q7. Thus, Q7's base current is proportional to the difference in input and feedback voltages. It forms the first half of a compound (Darlington-like) pair along with Q8, a 160V high-gain transistor. A 2.2k Ω resistor between its base and emitter speeds up switch-off.

Q7 and Q8 together form the Voltage Amplification Stage (VAS). Q8 has a constant current source for its collector load, comprising transistors Q6 and Q9. Together, these set the collector current for Q8 at around 6.5mA. As a result, the current flow to the base of Q7 is translated linearly to a voltage at Q8's collector which controls the output stage.

PNP transistor Q5 provides a constant current of around 2mA to the input pair and both it and Q9 are driven by Q6, which is set up to maintain a

constant voltage across their emitter resistors. In other words, Q6 biases the bases of Q5 and Q9 in such a way as to maintain an essentially static current through their collector/emitter junctions.

Output stage

The output stage consists of two pairs of Fairchild power transistors arranged as complementary emitter-followers. NPN transistors Q13 and Q14 are connected in parallel and source current for the speaker while Q15 and Q16 are PNP types and sink current from the speaker.

Surface-mount 3-watt 0.1 Ω 1% emitter resistors ensure equal current sharing, linearise the output stage and produce a small amount of local feedback. They also serve as handy shunts


for measuring the quiescent current.

Large power transistors require a substantial base current due to limited gain and this is supplied by driver transistors Q11 and Q12. These effectively make the output stage a complementary Darlington.

The parallel 220 Ω resistor and 220nF capacitor between the driver emitters speed up their switch-off when drive is being handed off from one to the other.

Quiescent current stabilisation

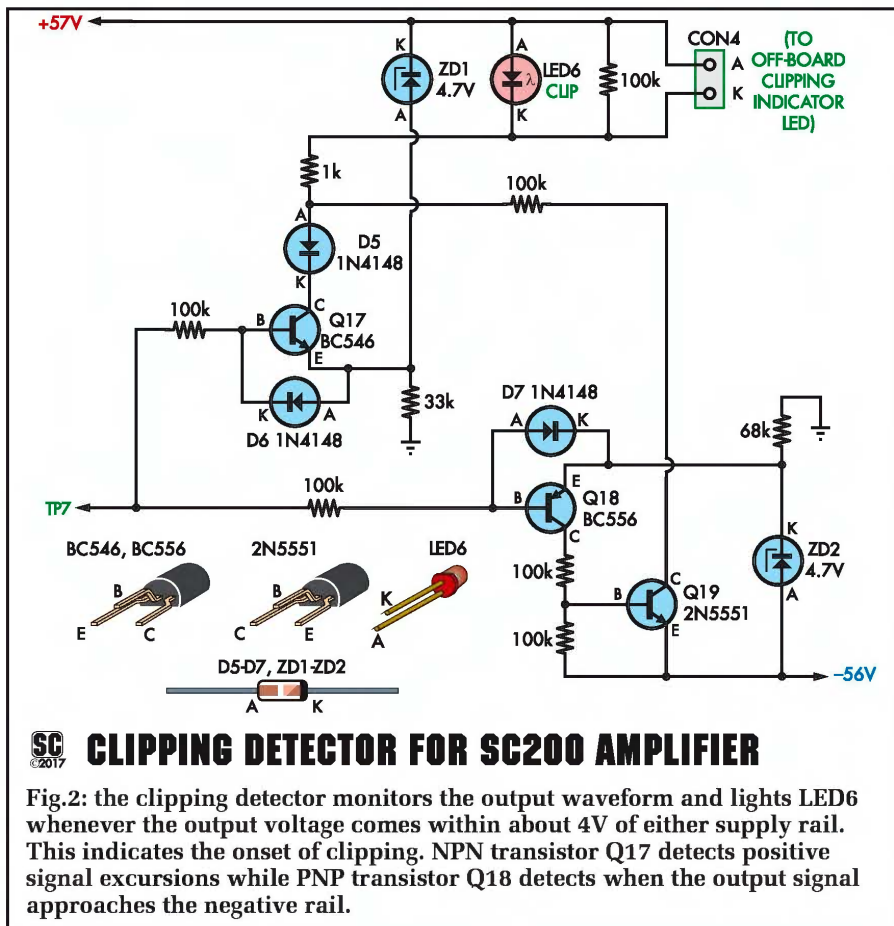The four base-emitter junctions in the output stage, plus the voltage across the emitter resistors adds up to around 2.2V (as shown just to the left of Q10 in the circuit diagram) and thus a similar DC bias must be maintained between the bases of Q11 and



Q12 to keep the output transistors in partial conduction most of the time; otherwise, there will be substantial crossover distortion each time the signal passes through 0V.

The reason is that when the signal polarity changes (ie, from positive to negative or vice versa), the output current drive is handed off from one set of output transistors to the other; ie, from Q13 and Q14 to Q15 and Q16 or the other way around.

This transition has to be smooth or

else there will be a step in the output voltage and the way to smooth it is to ensure that there is overlap between the conduction of both pairs.

In other words, with the output at zero volts, all four transistors are passing some current. This is known as the quiescent current.

This partial conduction requirement is a defining characteristic of a Class-AB amplifier (otherwise, they would be Class-B).

To maintain a more-or-less constant

quiescent current we need a “floating” voltage source of 2.2V between the bases of Q11 and Q12 and this is provided by the V_{BE} multiplier Q10 and its associated components.

But since the base-emitter voltages of the six transistors in the output stage all vary with temperature, a fixed floating voltage source is not suitable.

The base-emitter voltages drop with increasing temperature at around 2mV/°C so a fixed voltage source of 2.2V would lead to increased current as the output transistors heated up and ultimately, to thermal runaway and destruction.

V_{BE} multiplier

So our floating voltage source must not only be adjustable, to compensate for manufacturing variations in the output transistors and emitter resistors, it must also automatically reduce the bias as the amplifier heats up, so that the quiescent current remains reasonably constant.

But first, let’s explain the basic concept of a “ V_{BE} multiplier” before we consider how it tracks and adjusts for changes in operating temperature.

The V_{BE} multiplier is sometimes referred to as an “amplified diode” and this gives some insight into its operation. Consider that the base-emitter voltage of a conducting transistor is around 0.6V. The bias network to our V_{BE} multiplier comprises the 680Ω resistor between collector and base and the 1kΩ trimpot and 150Ω resistor between base and emitter. This forms a divider between its collector and emitter, with a tap at the base.

We already know that the voltage between base and emitter is 0.6V and

Specifications

Output power (230VAC mains): 200W RMS into 4Ω, 135W RMS into 8Ω
Frequency response (10Hz-20kHz): +0,-0.05dB (8Ω); +0,-0.12dB (4Ω);
Input sensitivity: 1.26V RMS for 135W into 8Ω; 1.08V RMS for 200W into 4Ω
Input impedance: 11.85kΩ shunted with 1nF
Rated Harmonic Distortion (4Ω, 8Ω): <0.01%, 20Hz-20kHz, 20Hz-30kHz bandwidth
Signal-to-Noise Ratio: -116dB unweighted with respect to 135W into 8Ω(20Hz-20kHz)
Damping factor: ~250
Stability: unconditionally stable with any nominal speaker load ≥4Ω
Music power: 170W (8Ω), 270W (4Ω)
Dynamic headroom: 1dB (8Ω), 1.3dB (4Ω)
Power supply: ±57V DC from a 45-0-45 transformer
Quiescent current: 88mA nominal
Quiescent power: 10W nominal
Output offset: typically <10mV untrimmed; <1mV trimmed

Parts list – SC200 Amplifier Module

- 1 double-sided PCB, coded 01108161, 117 x 84mm
- 1 diecast heatsink, 200 x 75 x 28mm (Altronics H-0536)
- 4 M205 fuse clips (F1,F2)
- 2 6.5A fast-blow M205 fuses (F1,F2)
- 1 small ferrite bead (FB1)
- 1 2.2μH air-cored inductor (L2)
(or 1 20mm OD x 10mm ID x 8mm bobbin and 1m of 1.25mm diameter enamelled copper wire, plug 10mm length of 20mm diameter heatshrink tubing)
- 1 1kΩ 25-turn vertical trimpot (VR1)
- 1 100Ω mini horizontal trimpot (VR2)
- 1 switched horizontal RCA socket (CON1) OR
- 1 2-pin polarised header (CON5) OR
- 1 vertical RCA socket (CON6)
- 1 4-way pluggable terminal block with socket, Dinkle 4EHDV or equivalent (CON2)
- 1 4-way pluggable terminal block with socket, Dinkle 3EHDV or equivalent (CON3)
- 4 TO-3P insulating washers
- 3 TO-126 or TO-220 insulating washers
- 7 15mm M3 machine screws with nuts
- 6 6mm M3 machine screws with nuts
- 4 9mm M3 tapped nylon spacers
- 8 PCB pins (optional; TP1-TP7)

Semiconductors

- 2 FJA4313 250V 17A NPN transistors, TO-3P (Q13,Q14)
- 2 FJA4213 250V 17A PNP transistors, TO-3P (Q15,Q16)
- 3 KSC2690A medium power NPN transistor (Q8,Q10,Q11)
- 2 KSA1220A medium power PNP transistors (Q9,Q12)
- 3 BC546 NPN transistors (Q3,Q4,Q7)*
- 4 BC556 PNP transistors (Q1,Q2,Q5,Q6)*
- 1 blue 3mm or SMD 3216/1206 LED (LED1)
- 2 red 3mm or SMD 3216/1206 LEDs (LED2,LED4)
- 2 green 3mm or SMD 3216/1206 LEDs (LED3,LED5)
- 1 1N4148 small signal diode (D1)*
- 1 BAV21 high-speed signal diode (D2)*
- 2 FR307 3A fast-recovery diodes (D3,D4)

Capacitors

- 1 1000μF 6.3V electrolytic
- 1 100μF 63V electrolytic
- 1 47μF 35V electrolytic
- 3 47μF 25V electrolytic
- 2 220nF 50V multi-layer ceramic or MKT
- 1 100nF 250VAC MKP
- 4 100nF 63V/100V MKT
- 2 1nF 63V/100V MKT
- 1 150pF 250V C0G/NP0 ceramic or MKT/MKP

Resistors (all 0.25W, 1% unless otherwise specified)

- 1 1MΩ 4 47kΩ 1 22kΩ 2 12kΩ 2 6.8kΩ 3 2.2kΩ 1 680Ω
- 1 470Ω 1W 5% through-hole or SMD 6332/2512
- 1 470Ω 1 330Ω 3 220Ω 1 120Ω
- 1 100Ω 1W 5% through-hole or SMD 6332/2512
- 2 100Ω 2 68Ω 2 47Ω 1 10Ω
- 1 6.8Ω 1% 3W SMD 6332/2512
- 4 0.1Ω 1% 3W SMD 6332/2512

** SMD versions
can be substituted;
see text next month*

since the beta (DC current gain) of the transistor is quite high (>100), it will draw negligible base current, so the current through the two resistors and trimpot VR1 will essentially be identical. Furthermore, since we will have 0.6V between base and emitter, it follows that we need 1.6V between collector and base, if we are to obtain 2.2V between collector and emitter.

So, to adjust the resistance of VR1 to obtain 1.6V between collector and emitter, we need a resistance ratio between collector/base and base/emitter of $1.6V \div 0.6V$ or 2.6666:1. This means the total resistance of VR1 and its series 150Ω resistor will be $680\Omega \times 0.6 \div 1.6 = 255\Omega$. And that means that trimpot VR1 must be set to a value of $255\Omega - 150\Omega = 105\Omega$.

We can therefore calculate the total resistance of the divider between collector and emitter at around $255\Omega + 680\Omega = 935\Omega$ and therefore $2.2V / 935\Omega = 2.35mA$ will flow through it.

The remainder of the 6.5mA, ie, 4.15mA must flow through the collector/emitter junction of Q10.

But what if the external operating conditions around the V_{BE} multiplier act to increase the voltage between its collector and emitter above 2.2V? If that did happen, the resistive divider would cause its base-emitter voltage to increase but that would force the transistor to turn on harder and that would have the effect of reducing the collector-emitter voltage.

So the V_{BE} multiplier transistor is instead forced to operate with a constant collector-emitter voltage! In other words, it operates as a shunt voltage regulator, maintaining a constant voltage across the collector/emitter

Additional parts for clipping detector circuit

- 1 2-pin header and matching plug (optional; CON4)

Semiconductors

- 1 BC546 NPN transistor (Q17)*
- 1 BC556 PNP transistor (Q18)*
- 1 2N5551 high-voltage NPN transistor (Q19)
- 1 yellow, amber or red LED (LED6)
- 2 4.7V 0.4W/1W zener diodes (ZD1,ZD2)*
- 3 1N4148 small signal diode (D5-D7)*

Resistors (all 0.25W, 1%)

- 6 100kΩ 1 68kΩ 1 33kΩ 1 1kΩ

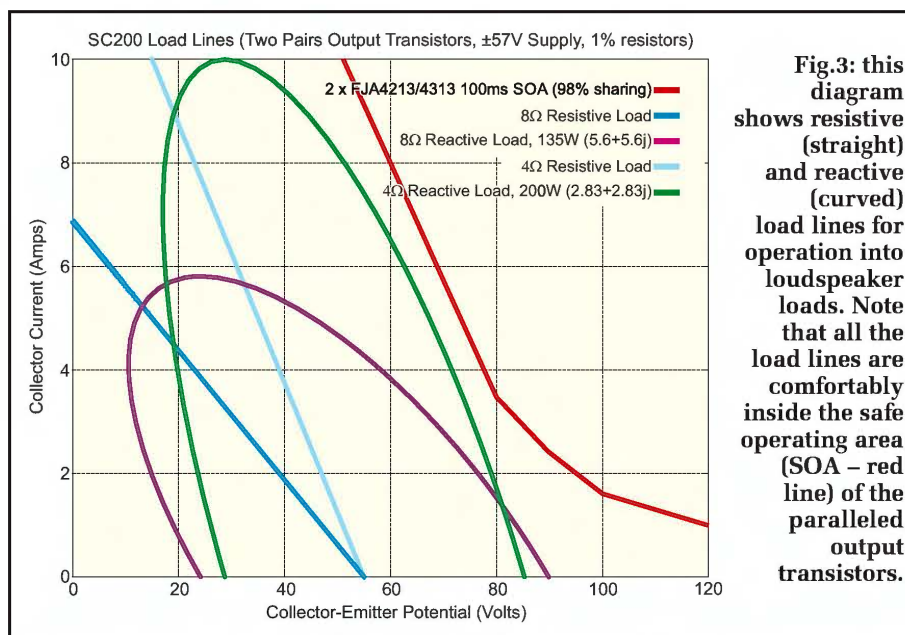


Fig.3: this diagram shows resistive (straight) and reactive (curved) load lines for operation into loudspeaker loads. Note that all the load lines are comfortably inside the safe operating area (SOA - red line) of the paralleled output transistors.

junction even if the current passing through it varies (but as long as it's higher than the 2.35mA required for the divider to operate properly).

Thermal tracking

So how does V_{BE} multiplier transistor Q10 adjust for temperature changes in the output transistors? We make it do that by mounting Q10 on the heatsink immediately between driver transistors Q11 and Q12. Furthermore, Q10 is the same transistor type as Q12, so the thermal tracking of the driver transistors and by extension, that of the four output power transistors, is quite good; not perfect but quite good.

So if the temperature of the heatsink rises by 50°C, that would mean that the required base-emitter voltages of all seven transistors (for a given collector current) on the heatsink will reduce by $50 \times 2\text{mV} = 100\text{mV}$.

If the base-emitter voltage of Q10 has reduced by 100mV, given that it operates with a gain of $(1.6 + 0.6) \div 0.6 = \sim 3.7$ times, the voltage of our floating source will be reduced to $2.2\text{V} - 100\text{mV} \times 3.7 = 1.83\text{V}$ and this voltage will be applied across the four base-emitter junctions of the complementary Darlington output stage transistors. That means that even though the transistor junction temperatures may have increased by 50°C, their quiescent current should remain much as it was at much lower temperatures.

In practice, the process is not quite that good so we also have local feedback provided by the 0.1Ω 3W emitter resistors for the output transistors. If

the voltage across these emitter resistors increases, due to increasing quiescent current, that will tend to reduce the base-emitter voltage (by subtraction) and therefore the current will reduce (or at least, not increase by as much as it would without them).

By the way, the 220Ω resistors between either end of the V_{be} multiplier Q10 and Q11/Q12 act as RF stoppers and also limit current flow under fault conditions (eg, a short circuit).

Feedback & compensation

Negative feedback goes from the junction of the output emitter resistors to the base of Q2 via a 12kΩ/470Ω resistive divider, setting the closed loop gain to 25.5 times (+28.5dB). The bottom end of the feedback network is connected to ground via a 1000µF electrolytic capacitor.

This has a negligible effect on low-frequency response but sets the DC gain to unity, so that the input offset is not magnified at the output by the gain factor of 25.5.

The 150pF compensation capacitor is connected between the collector of Q8 and the base of Q7, ie, it is effectively a Miller capacitor for the VAS "Darlington" (in a real Darlington, the collectors would be common). This is a single-pole compensation arrangement which rolls off the open-loop gain at a high frequency to give unconditional stability with highly reactive loads across the amplifier's output.

The 22kΩ resistor in series with the collector of Q7 limits its current under fault conditions. Should the amplifier

outputs be shorted, it will try to pull the output either up or down as hard as possible, depending on the offset voltage polarity.

If it tries to pull it up, the output current is inherently limited by the approximate 6.5mA current source driving Q11 from Q9. However, if it tries to pull down, Q8 is capable of sinking much more than 6.5mA.

The 22kΩ resistor limits Q8's base current to around 2mA and since Q8 has a beta of around 120, Q8's collector will not sink much more than 240mA. This is still enough to burn out Q12's 220Ω base resistor but that may be the only damage from an extended short circuit; very brief short circuits will should not cause any lasting damage.

Note that the 22kΩ resistor will cause Q7's collector voltage to drop as it is called on to supply more current and the Early effect means its gain will drop when this happens. This can cause local negative feedback and oscillation. A low-value capacitor in parallel with the 22kΩ resistor prevents this while still allowing the current to Q8's base to quickly drop to 2mA during a short circuit.

Output filter

The 0.1Ω 3W emitter resistors of output transistors Q13-Q16 are connected to the output at CON3 via an RLC filter comprising a 2.2µH series inductor in parallel with a 6.8Ω 3W surface-mount resistor, with a 100nF capacitor across the output terminals. The inductor isolates any added capacitance at the output (eg, from the cables or the speaker's crossover network) from the amplifier at high frequencies, which could otherwise cause oscillation. The resistor reduces the inductor's Q, to damp ringing and also forms a Zobel network in combination with the 100nF capacitor, which also aids stability.

Driving a line transformer

While a very low output offset voltage gives slight benefits when driving normal speakers, it's absolutely critical when driving a 100V line transformer (for professional PA applications) or electrostatic speaker (which will typically have an internal transformer).

That's because the DC resistance of the primary winding will be much lower than that of a loudspeaker's voice coil, so a lot of DC current can flow with an output offset voltage of

WARNING!

High DC voltages (ie, $\pm 57V$) are present on this amplifier module. In particular, note that there is 114V DC between the two supply rails. Do not touch any wiring (including the fuseholders) when the amplifier is operating, otherwise you could get a lethal shock.

just a few millivolts.

The other requirement for driving a transformer is to have protection diodes on the amplifier output to clamp inductive voltage spikes which occur when the amplifier is driven into clipping (overload).

These would otherwise reverse-bias the output transistor collector-emitter junctions, possibly causing damage. D3 and D4 are 3A relatively fast recovery diodes with low junction capacitance for their size and we have checked that they do not have any impact on performance.

So there should be no changes necessary to use this module in a PA amplifier or to drive electrostatic speakers, as long as the output offset voltage is trimmed out during set-up.

Indicator LEDs


We have already mentioned a blue LED1 connected in series with the input pair current source and which is lit while ever the board has power applied. Since there is an $\sim 50V$ drop required from Q5's collector to VR2's wiper, the power to operate this LED is effectively free.

We've also included red/green LEDs LED2-LED5 to indicate the status of the output stage power rails. It isn't always obvious that a fuse has blown without careful inspection.

In the case of LED2, assuming F1 has not blown, the voltage at either end of the fuse-holder is the same so no current will flow through the red junction. However, LED3 is connected between the collectors of Q11, Q13 and Q14 and ground via a 47k Ω current-limiting resistor, so it will light up.

If fuse F1 blows, the collector voltages will drop to near 0V, so green LED3 will turn off but the full rail voltage will be across the fuse-holder and so the red LED2 will switch on. Similarly, LED5/LED4 indicates green/red when F2 is OK/blown.

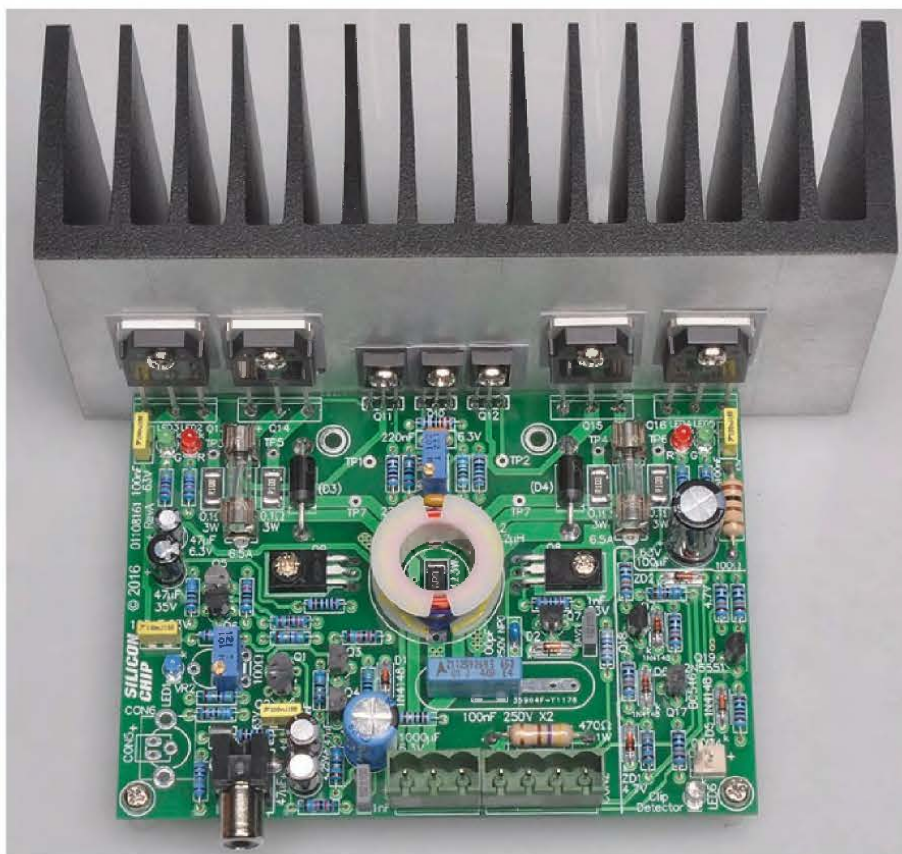These LEDs will also indicate if one of the two supply rails is missing (eg, due to a wiring fault); in this case,



Spot the five surface-mount 3W resistors. Four are the emitter resistors for the output transistors and the fifth is inside the output inductor.

LED1 will probably still light up so it might not otherwise be obvious.

Clipping indicators

Now we can talk about the on-board clipping detector/indicator circuit. This involves just a few components and will indicate whenever the amplifier is driven into clipping, which may not be obviously audible.

It can drive an external LED mounted on the front panel of the amplifier. These components may be omitted if they are not required.

The clipping detector circuit is shown in Fig.2. Zener diode ZD1 derives a reference voltage 4.7V below the nominally 57V positive rail, ie, at about +52V. This is connected to the emitter of NPN transistor Q17. Its base is connected to the amplifier's output via a 100k Ω current-limiting resistor, with diode D6 preventing its base-emitter junction from being reverse-biased.

At the onset of clipping, the speaker voltage will rise above the +52V reference plus Q17's base-emitter voltage, ie, to about +53V. Q17 will switch on and sink current via LED4, a 1k Ω current-limiting resistor and isolating

diode D5, lighting up clipping indicator LED6. As the reference voltage is relative to the positive rail, any variations in supply voltage will be accounted for.

ZD2, PNP transistor Q18 and diode D7 work in an identical manner for negative excursions.

However, Q18 drives LED6 via high-voltage NPN transistor Q19 which acts as a level shifter. The 100k Ω resistor in series with its collector limits the LED current to a similar level (1mA) despite the much higher rail voltage differential.

This is not the simplest clipping detector circuit but it presents an almost completely linear load to the amplifier output, to minimise the possibility of any distortion due to its input load current.

It's connected to the driven end of L2, to give the amplifier the best chance to cancel out any non-linearities in the load it introduces.

Next month

Have we whetted your collective appetites? Next month we will present the full details of performance and construction details.