

# BRUTUS 170W / S

stereo power amplifier

BRUTUS - 170W/S is stronger brother of the popular BRUTUS - 100W/S power amplifier. BRUTUS - 170W/S is operating in the bridge configuration, which ensures such a high output.

Thanks to IC TDA7294 manufactured by SGS Thompson (www.st.com) that you can buy for few Euros you can make a compact 170W power amplifier. It's PCB measures just 5,5 x 21 cm.

TDA7294 is housed in Multiwatt 15 package and is intended for audio power amplifiers operating in class AB. It's usable in wide area of applications, from Home Cinema speaker systems to active speakers, high-end TV sets and of course home brew amplifier projects. Due to it's large power supply voltage range is this IC capable of delivering large power to 4, 8 and 16 Ohms speakers. TDA7294 has 100W output power at RL = 8 Ohms; VS = ± 38V, and 100W at RL = 4 Ohms; VS = ± 29V. THD is lower than 0,1% at PO = 0.1 to 50W and f = 20Hz to 20kHz. Detailed information on power output and THD can be seen in diagrams.

Let us firstly list basic data about TDA7249 in table 1. Special attention should be paid for the max. power supply voltage which should not ex-

Symbol	Parameter	Value	Unit
Vs	Supply voltage (no signal)	± 50V max	V
Io	Output peak current	10	A
Ptot	Power dissipation Tcase= 70 °C	50	W
Top	Operating ambient temperature range	0 to + 70	°C

Table 1: Absolute maximum ratings

ceed ± 49V. In case that voltage exceeds ± 49V your TDA7294 will silently burn out. In the amplifier circuit are four pieces of TDA7294. It means that we might find out that all four ICs are dead as Dodo! Take a look also at table 2, where technical data for TDA7294 are listed.

Another important issue is speaker impedance. Speaker should have min. 8 Ohms impedance. Just for illustration, with Vss of just ± 25V and 8 Ohms speakers output power reaches 150W, while at Vss = ± 35V and 16 Ohms speaker we can reach output power of respectable 170W! You may ask yourself what can happen if instead of 8 Ohms speakers 4 Ohms ones are used? Well, not much if TDA7294 is concerned. Amplifier will deliver max. output power to 4 Ohms speakers limited time until ICs overheat. Due to IC's thermal protection circuitry TDA7294 will automatically reduce output power to safe value. Schematic diagram of the BRUTUS - 170W/S power amplifier can be seen at fig. 2

## DMOS 170W schematic


As mentioned earlier, BRUTUS - 170W/S is configured in the bridge configuration. One of it's advantages is that there is no output capacitor which improves frequency response of amplifier. With the switch S1 MUTE or

**ELECTRICAL CHARACTERISTICS** (Refer to the Test Circuit  $V_S = \pm 35V$ ,  $R_L = 8\Omega$ ,  $G_V = 30dB$ ;  $R_G = 50\Omega$ ;  $T_{amb} = 25^\circ C$ ,  $f = 1\text{ kHz}$ ; unless otherwise specified.)

Symbol	Parameter	Test Condition	Min.	Typ.	Max.	Unit
Vs	Supply Range		±10		±40	V
Iq	Quiescent Current		20	30	60	mA
Ib	Input Bias Current				500	nA
Vos	Input Offset Voltage				±10	mV
Ios	Input Offset Current				±100	nA
PO	RMS Continuous Output Power	d = 0.5%; Vs = ± 35V, RL = 8Ω Vs = ± 31V, RL = 6Ω Vs = ± 27V, RL = 4Ω	60	70		W
	Music Power (RMS)	d = 10% IEC268.3 RULES - Δt = 1s (*) RL = 8Ω; VS = ±38V RL = 6Ω; VS = ±33V RL = 4Ω; VS = ±29V (***)		100	100	W
	Total Harmonic Distortion (**)	PO = 5W; f = 1kHz PO = 0.1 to 50W; f = 20Hz to 20kHz Vs = ±27V, RL = 4Ω; PO = 5W; f = 1kHz PO = 0.1 to 50W; f = 20Hz to 20kHz		0.005	0.1	%
SR	Slow Rate		7	10		V/μs
Gv	Open Loop Voltage Gain			80		dB
Gv	Closed Loop Voltage Gain		24	30	40	dB
on	Total Input Noise	A = curve f = 20Hz to 20kHz		1	5	μV
fL, fH	Frequency Response (-3dB)	PO = 1W				20Hz to 20kHz
RI	Input Resistance		100			kΩ
SVR	Supply Voltage Rejection	f = 100Hz; Vripple = 0.5Vrms	60	75		dB
TS	Thermal Shutdown			145		°C
<b>STAND-BY FUNCTION (Ref: -Vs or GND)</b>						
VST on	Stand-by on Threshold				1.5	V
VST off	Stand-by off Threshold		3.5			V
ATT on-by	Stand-by Attenuation		70	90		dB
Iq at-by	Quiescent Current @ Stand-by			1	3	mA
<b>MUTE FUNCTION (Ref: -Vs or GND)</b>						
VMT on	Mute on Threshold				1.5	V
VMT off	Mute off Threshold		3.5			V
ATT mute	Mute Attenuation		60	80		dB

Note (\*): MUSIC POWER CONCEPT MUSIC POWER is the maximal power which the amplifier is capable of producing across the rated load resistance (regardless of non linearity) 1 sec after the application of a sinusoidal input signal of frequency 1kHz.  
Note (\*\*): Tested with optimized Application Board (see fig. 2)  
Note (\*\*\*): Limited by the max. allowable current.

Table 2: Electrical characteristics

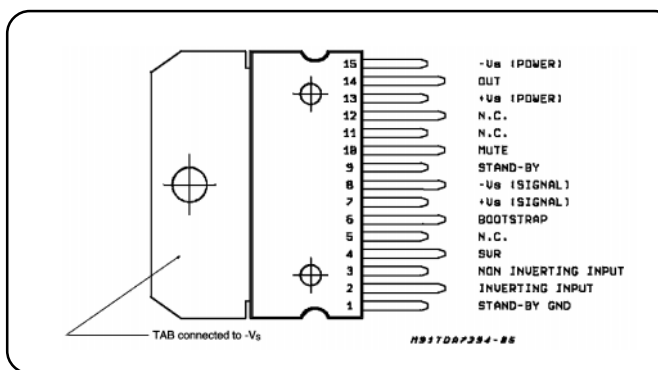

PLAY mode are selected.

Let us now take a look at IC itself. TDA7294 has 4 main parts: MUTE circuitry with Stand-by function, preamplifier circuitry, power output stage and short protection circuitry. TDA7294 has built-in protection from the short circuit on the out-

put terminals. It has also thermal protection which turns off output stage, when silicon die reaches 145°C.

Power supply is blocked with 100nF capacitors near ICs. Together with 2.200 μF filter capacitors ensures a clean power supply voltage for IC. Let us emphasize that 2.200 μF capacitors that are placed near IC are here purely to improve 100 Hz filtering while main filtering must be done with 10.000 μF capacitors that are located on power supply PCB.

Resistors R2 and R3 (R12 and R15 respectively) set the amplification of the circuit. With values that you see in the schematic diagram amplification is set to 30 dB. Capacitor C9 sets the low frequency cut-off therefore lowering value of C9 should be done carefully. If you lower capacitance of C9 the low frequency cut-off will be higher which means that lower tones will be attenuated. Lowering capacitance of decoupling capacitor C3 will cause same effect as changing value of C9. Input resistance is set with R1, which should be same as R2. Electrical schematic of BRUTUS - 170W/S is a bit different from the original application note. Difference is at the MUTE and STAND-BY pins, that are connected to one switch S1.

To reach max. attenuation MUTE switch S1 should be connected to GND, while for normal operation it should be connected to +Vcc.

## Power supply

Power supply of this amplifier is simple. You should use centre-tapped transformer with 2x27V AC


**APPLICATION SUGGESTIONS** (see Test and Application Circuits of the Fig. 1)  
 The recommended values of the external components are those shown on the application circuit of Fig. 1. Different values can be used; the following table can help the designer.

COMPONENTS	SUGGESTED VALUE	PURPOSE	LARGER THAN SUGGESTED	SMALLER THAN SUGGESTED
R1 (*)	22k	INPUT RESISTANCE	INCREASE INPUT IMPEDANCE	DECREASE INPUT IMPEDANCE
R2	680Ω	CLOSED LOOP GAIN SET TO 30dB (**)	DECREASE OF GAIN	INCREASE OF GAIN
R3 (*)	22k		INCREASE OF GAIN	DECREASE OF GAIN
R4	22k	ST-BY TIME CONSTANT	LARGER ST-BY ON/OFF TIME	SMALLER ST-BY ON/OFF TIME; POP NOISE
R5	10k	MUTE TIME CONSTANT	LARGER MUTE ON/OFF TIME	SMALLER MUTE ON/OFF TIME
C1	0.47μF	INPUT DC DECOUPLING		HIGHER LOW FREQUENCY CUTOFF
C2	22μF	FEEDBACK DC DECOUPLING		HIGHER LOW FREQUENCY CUTOFF
C3	10μF	MUTE TIME CONSTANT	LARGER MUTE ON/OFF TIME	SMALLER MUTE ON/OFF TIME
C4	10μF	ST-BY TIME CONSTANT	LARGER ST-BY ON/OFF TIME	SMALLER ST-BY ON/OFF TIME; POP NOISE
C5	22μF	BOOTSTRAPPING		SIGNAL DEGRADATION AT LOW FREQUENCY
C6, C8	1000μF	SUPPLY VOLTAGE BYPASS		DANGER OF OSCILLATION
C7, C9	0.1μF	SUPPLY VOLTAGE BYPASS		DANGER OF OSCILLATION


(\*) R1 = R3 FOR POP OPTIMIZATION

(\*\*) CLOSED LOOP GAIN HAS TO BE ≥ 24dB


Table 3: The recommended values of the external components (refers to original application note at fig. 1)

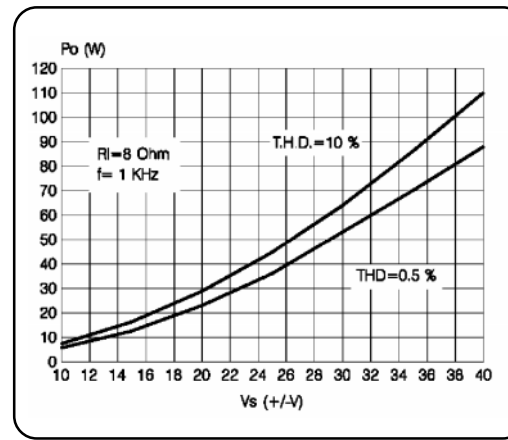

Figures 3: Output Power vs. Supply Voltage.

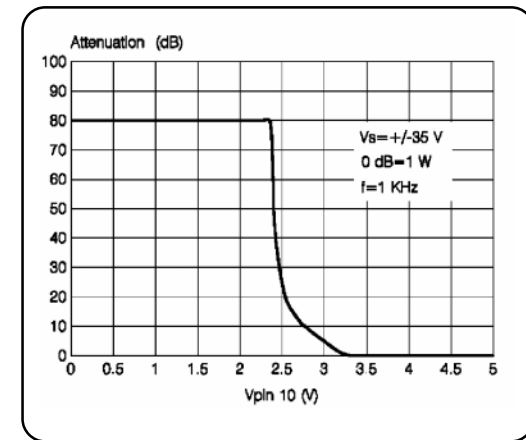

Figures 5: Diagram of MUTE function

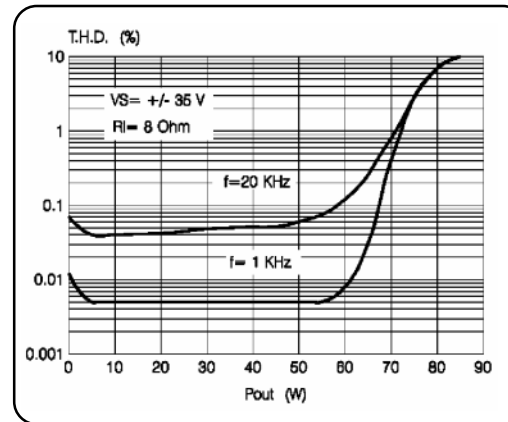

Figures 3: Distortion vs. Output Power

mer we recommend to make a simple circuit as indicated in the schematic diagram (figure 2). The circuit consists of resistor RS and switch S2. Resistor should have 390 Ohms/ 2W. At powering up the amplifier resistor limits inrush current to a safe value. Few seconds after turning power on you can close switch S2 which will enable normal operation of amplifier. All of you that are good in electronics will probably make a time relay, which will automatically after few seconds short resistor RS. In case that you do not wish to use this simple protective circuit you will probably change fuses quite often. On Fig. 6 you can see schematics of simple time delay circuit. This circuit can be built on prototype veroboard. In the circuit the BS170 N-type MOSFET transistor is used. To it's Gate the capacitor Cs is connected. Cs together with Rs makes an RC circuit, which determines time delay, at which transistor T1 will turn on relay. Resistor Rp determines discharge time of Cs. This resistor is here because Cs cannot discharge itself through MOSFET due to high input resistance of Gate terminal. If Cs would not discharge, T1 would remain open also when we turn off power supply, which would mean that at next powering up the RS will be shorted and will not function as a protection for your transformer. Zener diode D1 is needed to drop supply voltage to a safe value. Instead of zener diode

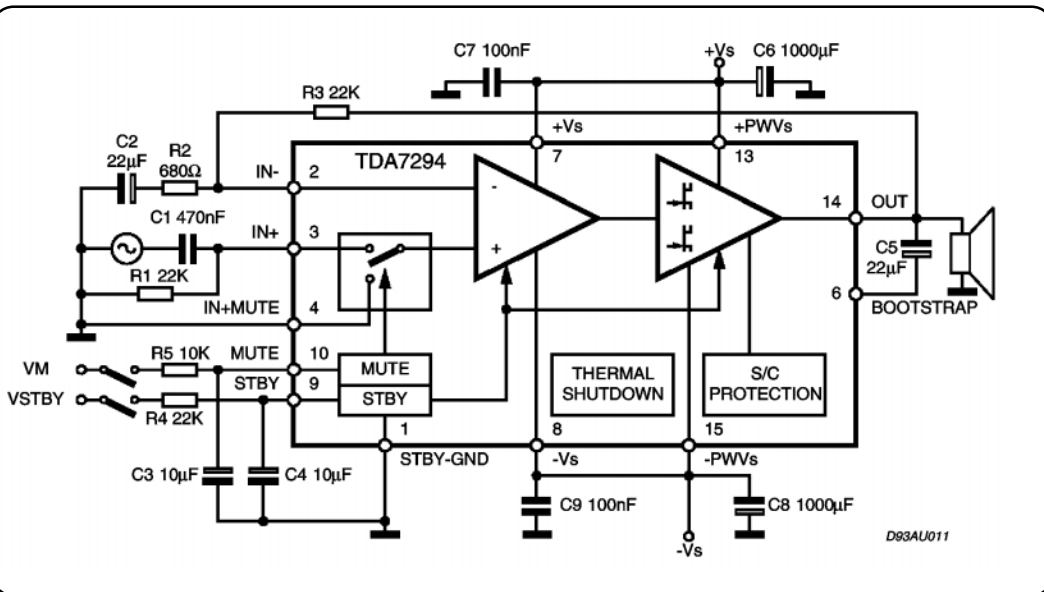


Figure 1: Typical application circuit

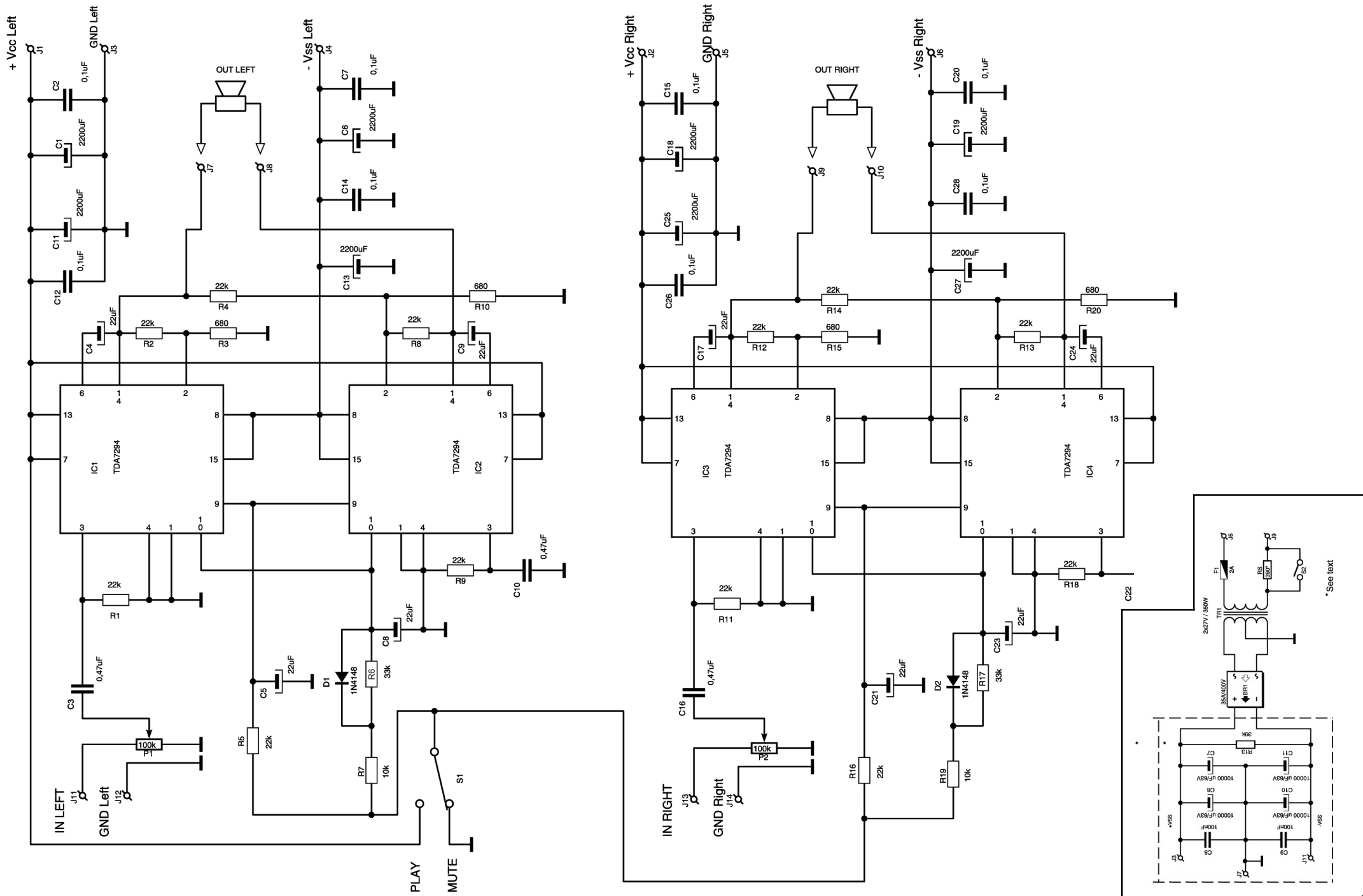


Fig. 2: Schematic of the BRUTUS - 170W/S power amplifier

Pieces	Value	Reference
2	Diode 1N4148	D1, D2
4	IC TDA7294	IC1 - IC4
8	Capac. 2.200 $\mu$ F / 50V	C1, C6, C11, C13, C18, C19, C25, C27
8	Capac. 22 $\mu$ F / 63V	C4, C5, C8, C9, C17, C21, C23, C24
8	Capac. 100 nF / 50V	C2, C7, C12, C14, C15, C17, C20, C28
4	Capac. 470 nF / 50V	C3, C10, C16, C22
2	Power terminal block 3 pin	J1, J2, J7, J8, J9, J10
4	Power terminal block 2 pin	J3, J4, J5, J6, J11, J12, J13, J14
1	PCB DMOS 170W	PCB
2	Resistor 10k / 1/4W	R7, R19
12	Resistor 22k / 1/4W	R1, R2, R4, R5, R8, R9, R11, R12, R13, R14, R16, R18
2	Resistor 33k / 1/4W	R8, R17
4	Resistor 680E / 1/4W	R3, R10, R15, R20

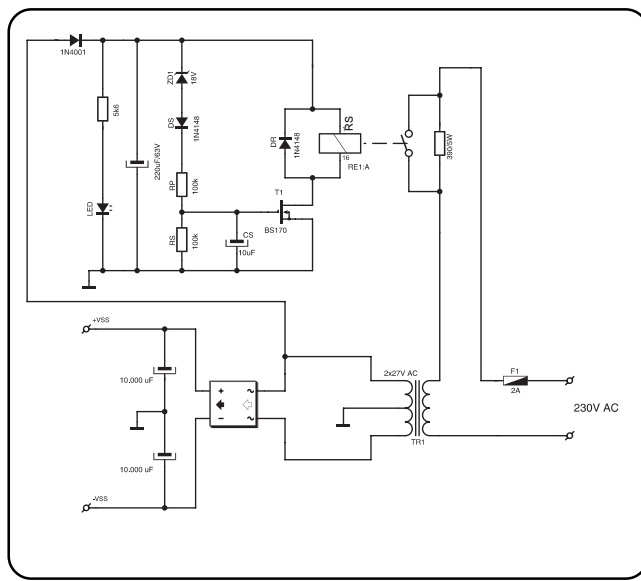


Figure 6: Time delay circuit

de you can use 12V regulator like 7812. Power supply of time delay circuit is connected to 27V AC and GND as seen in the schematic diagram. LED is added to signalize power supply voltage.

Table 4: Table of components for BRUTUS - 170W/S stereo amplifier with TDA7294

## Building Power amplifier KIT


Building power amplifier is easy. Firstly solder all resistors, diodes and ceramic capacitors. Then solder small electrolytic capacitors, connectors, sockets and finally 2.200  $\mu$ F capacitors. If you feel more comfortable you may firstly screw all TDA7294 to suitable heatsink and the solder them to the PCB. At mounting TDA7294 to heatsink note that you should use suitable mica washers to isolate ICs from the potential of the enclosure - which is normally connected to GND. Tabs of TDA7294 are connected to -Vss so you should be careful when mounting them to heatsink. Screws should be insulated with insulating bushes. Between mica washer and TDA7294 you should apply silicone heatsink compound which improves thermal conductivity between TDA7294 and heatsink. Suitable mica washers and insulating bushes are included in the KIT set.

When screws are screwed (do not screw them too much - you might damage TDA7294!!) you should check resistance between TDA7294 tab and heatsink with continuity check with your measuring instrument. If there is no connection you may mount heatsink to your enclosure. Before you connect power supply to your amplifier make sure that input potentiometers (P1 and P2) are connected to GND i.e. input signal is set at minimum.

We have got reports from customers that when they turned on power supply, amplifier delivered max. output power to loudspeakers which caused damage of loudspeakers. When you turn on power supply with volume set to minimum you will not hear a thing - also due to automatic elimination of pop and click at power on.

TDA7294 has very minor noise, so do not be surprised if nothing will be heard. Also do not forget to turn MUTE/PLAY switch to PLAY position. Connect input signal to J11&J12 (J13&J14 respectively). Slowly turn on volume and now you could enjoy sound of your BRUTUS - 170W/S amplifier.

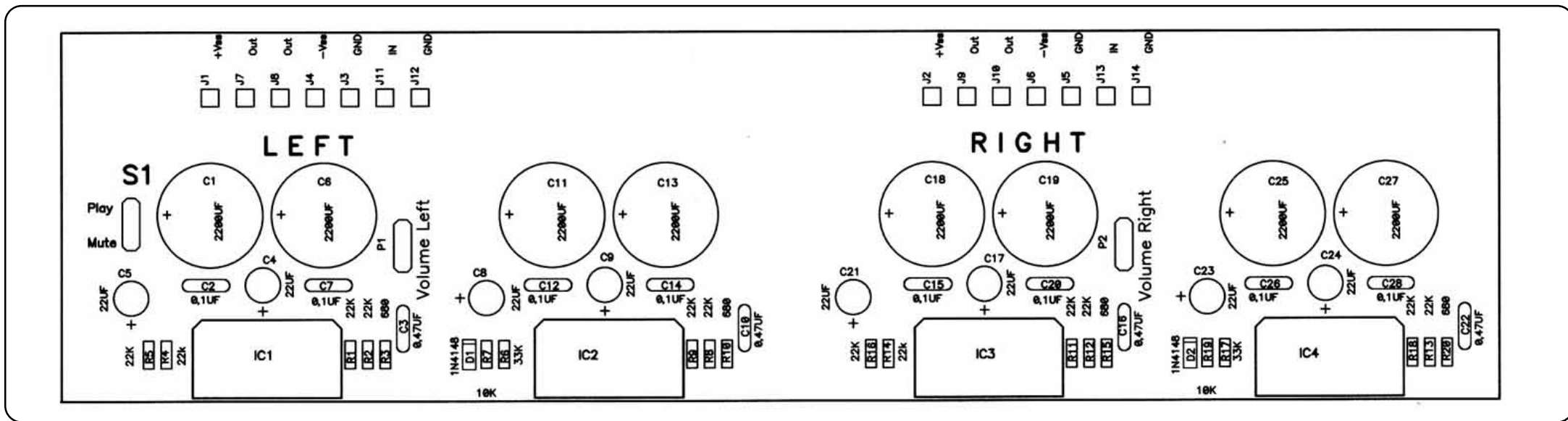should apply silicone heatsink compound which improves thermal conductivity between TDA7294 and heatsink. Suitable mica washers and insulating bushes are included in the KIT set.



P.C.B. and Components layout