

EE105 – Fall 2015

Microelectronic Devices and Circuits

Prof. Ming C. Wu
wu@eecs.berkeley.edu
511 Sutardja Dai Hall (SDH)



4-1



Imperfections in Practical Op-Amps


- Finite open-loop gain ($A_0 < \infty$)
- Finite input resistance ($R_i < \infty$)
- Non-zero output resistance ($R_o > 0$)
- Finite bandwidth
- Offset voltage
- Input bias and offset currents



4-2






Offset Voltage

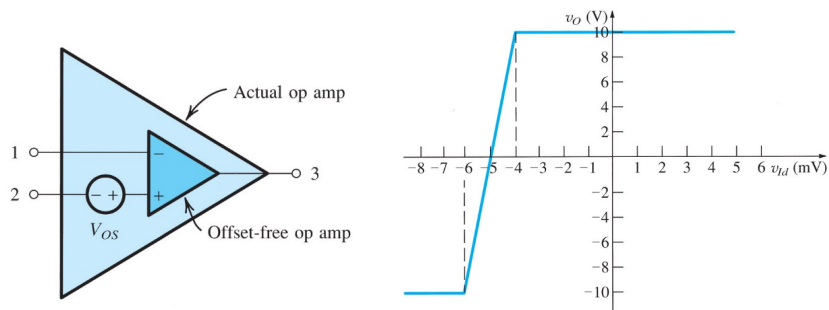

4-3



Trimming of Offset Voltage

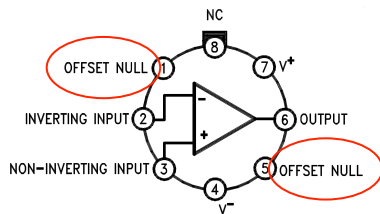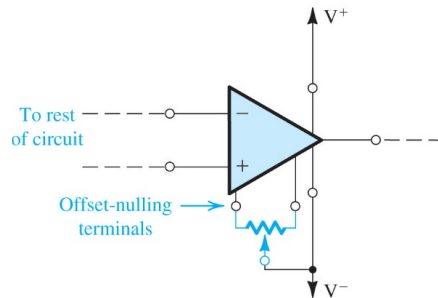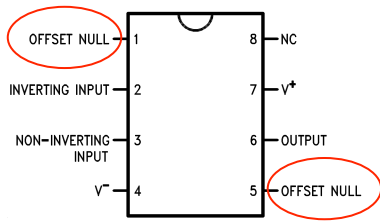


The output dc offset voltage of an op amp can be trimmed to zero by connecting a potentiometer to the two offset-nulling terminals. The wiper of the potentiometer is connected to the negative supply of the op amp.



4-4



Input Bias Currents and Offset Currents

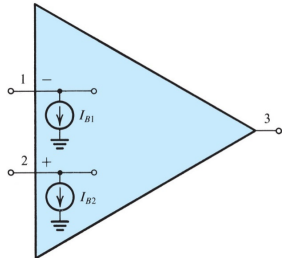

The input terminals need to be supplied with bias currents, I_{B1} and I_{B2} , for Op Amp to function. (This will become clear towards the end of the semester).

$$\text{Input bias current: } I_B = \frac{I_{B1} + I_{B2}}{2}$$


$$\text{Input offset current: } I_{OS} = |I_{B1} - I_{B2}|$$

Typical bipolar transistor Op amps:

$$I_B \sim 100 \text{ nA}$$

$$I_{OS} \sim 10 \text{ nA}$$

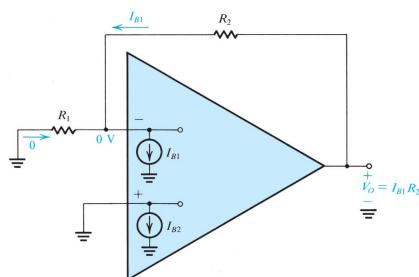
Effect of Input Bias Current in Amplifier Circuit



In the absence of input voltage, the output should be zero for ideal Op Amp. However, with non-zero I_B ,

$$V_O = I_{B1} R_2 \approx I_B R_2$$

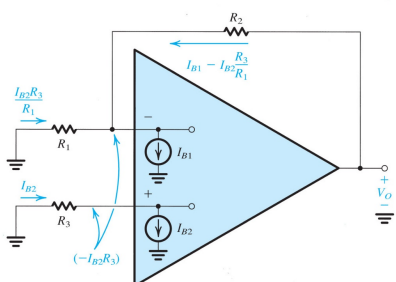Reducing the Effect of Input Bias Currents



$$V_O = -I_{B2}R_3 + R_2 \left(I_{B1} - \frac{I_{B2}R_3}{R_1} \right)$$

First approximate $I_{B1} = I_{B2} = I_B$

$$V_O = -I_B R_3 + I_B R_2 - \frac{I_B R_3}{R_1} R_2 = I_B \left(R_2 - R_3 \left(1 + \frac{R_2}{R_1} \right) \right)$$

$$\text{Choose } R_3 = \frac{R_2}{1 + \frac{R_2}{R_1}}, V_O = 0$$

Now consider $I_{B1} = I_B + \frac{I_{OS}}{2}$

$$\text{and } I_{B2} = I_B - \frac{I_{OS}}{2}$$


$$V_O = I_{OS} R_2$$



4-7



Frequency Response of Open-Loop Op Amp

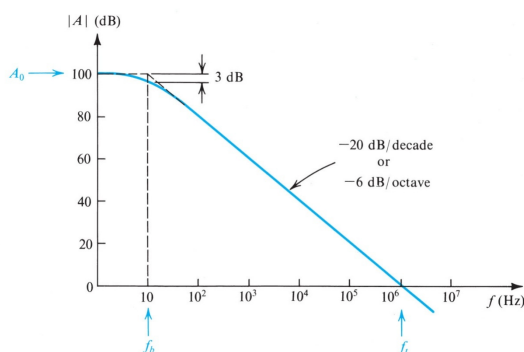

$$A(j\omega) = \frac{A_0}{1 + j\omega / \omega_b}$$

A_0 : dc gain

ω_b : 3dB frequency

$\omega_t = A_0 \omega_b$: unity-gain bandwidth
(or "gain-bandwidth product")

For high frequency, $\omega \gg \omega_b$

$$A(j\omega) = \frac{\omega_t}{j\omega}$$

Single pole response with a dominant pole at ω_b




4-8



Frequency Response of Closed-Loop Op Amp

Steps to find frequency response of closed-loop amplifiers:

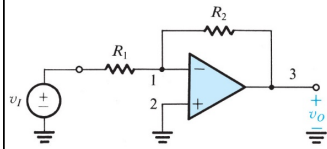1. Find the transfer function with finite open-loop gain. For example, for inverting amplifier:



$$G = \frac{v_o}{v_i} = \left(-\frac{R_2}{R_1} \right) \frac{1}{1 + \frac{1 + R_2/R_1}{A}}$$

2. Substitute A with $A(j\omega) = \frac{A_0}{1 + j\omega/\omega_b}$

3. Simplify the expression

$$G(\omega) = \left(-\frac{R_2}{R_1} \right) \frac{1}{1 + (1 + R_2/R_1) \frac{1 + j\omega/\omega_b}{A_0}}$$

$$= \left(-\frac{R_2}{R_1} \right) \frac{1}{1 + \frac{(1 + R_2/R_1)}{A_0} + \frac{j\omega}{\left(\frac{A_0\omega_b}{1 + R_2/R_1} \right)}}$$



4-9




Frequency Response of Closed-Loop Inverting Amplifier Example

$$G(\omega) \approx \left(-\frac{R_2}{R_1} \right) \frac{1}{1 + \frac{j\omega}{\omega_{3dB}}} \quad \text{where } \omega_{3dB} = \frac{A_0\omega_b}{1 + R_2/R_1}$$

Note:

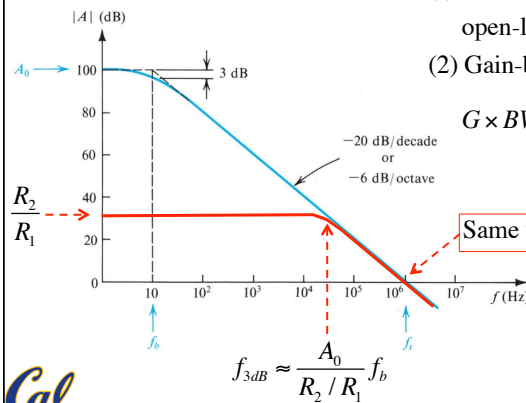- (1) 3-dB frequency is higher than open-loop bandwidth, ω_b
- (2) Gain-bandwidth product remains unchanged:

$$G \times BW = \frac{R_2}{R_1} \frac{A_0\omega_b}{1 + R_2/R_1} \approx \frac{R_2}{R_1} \frac{A_0\omega_b}{R_2/R_1} = A_0\omega_b = \omega_t$$




4-10



Output Saturation

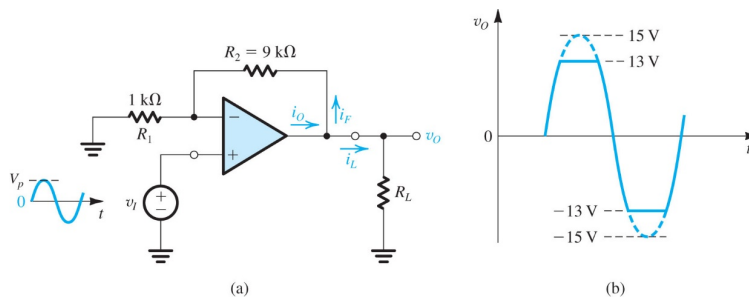- The output voltage swing is limited by
 1. Saturation voltage (usually a volt or two lower than power supply voltage)
 2. Maximum output current (in case of small load resistance)
- Output waveform appears to be “clipped” when either condition happens



Cal

4-11

BSAC

Slew Rate

Amplifier output is limited by "slew rate":
maximum rate of change possible at output



$$SR = \left. \frac{dv_o}{dt} \right|_{\max}$$

SR is specified in datasheet in $\text{V}/\mu\text{s}$.


Note

SR limit is different from bandwidth limit:

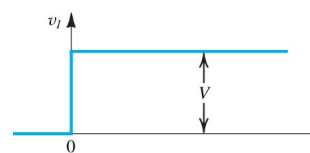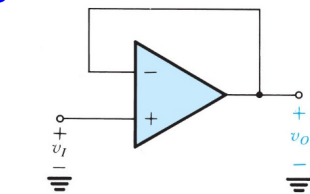- Limited bandwidth is a linear phenomenon, it does not change the shape of input sinusoid
- SR limitation can cause nonlinear distortion to input sinusoidal signal



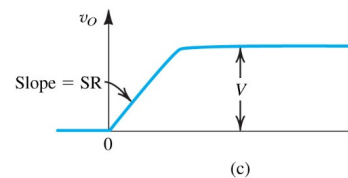Output not able to follow input;
Slope limited by SR




Cal

4-12


BSAC

Comparison of Slew Rate and Bandwidth Limits

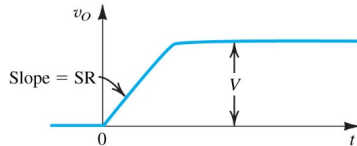For step function input waveform, both SR and bandwidth limits cause the output to rise with a finite slope, but there is an important difference:



Slew rate limited output:
Slope = SR

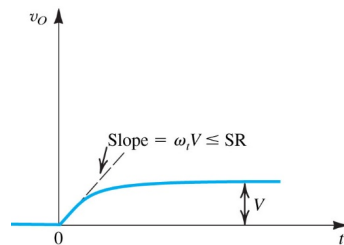


Bandwidth limited output:
Slope = $\omega_i V < SR$
(V is the steady state output voltage)



4-13



Full-Power Bandwidth

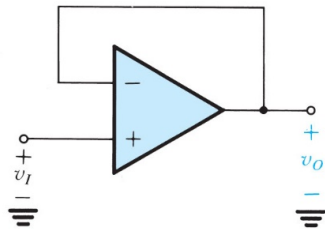

For sinusoidal input to unity-gain follower:

$$v_I = V_i \sin \omega t$$

Rate of change:


$$\frac{dv_I}{dt} = V_i \omega \cos \omega t \leq SR$$

Full-power bandwidth:

The frequency at which SR-limited distortion starts to occur for an output sinusoid with maximum rated output voltage, $V_{o\max}$,

$$\omega_M V_{o\max} = SR$$

$$f_M = \frac{SR}{2\pi V_{o\max}}$$

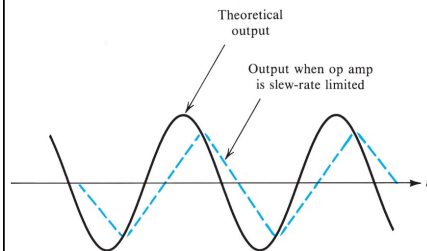

4-14

