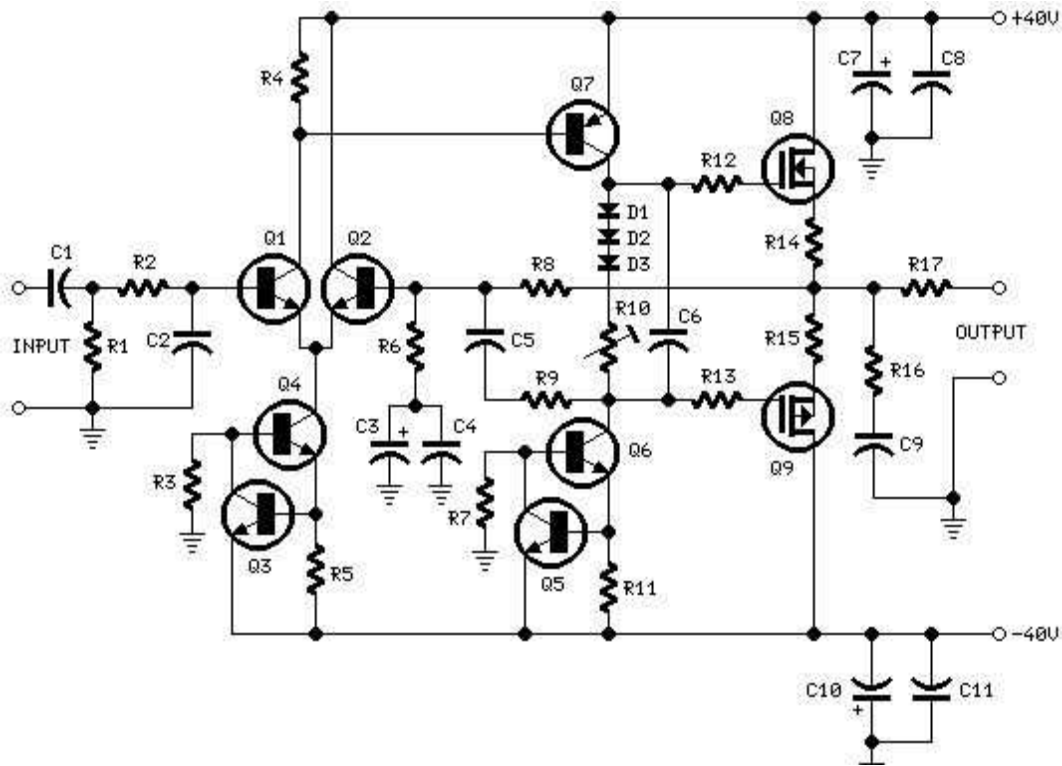


# AMPLIFICATOR AUDIO cu MOSFET 60W, 8 Ohmi, THD=0,01%.



## Part List:

R1 \_\_\_\_\_ 47K 1/4W Resistor  
 R2 \_\_\_\_\_ 4K7 1/4W Resistor  
 R3 \_\_\_\_\_ 22K 1/4W Resistor  
 R4 \_\_\_\_\_ 1K 1/4W Resistor  
 R5,R12,R13 \_\_\_\_ 330R 1/4W Resistors  
 R6 \_\_\_\_\_ 1K5 1/4W Resistor  
 R7 \_\_\_\_\_ 15K 1/4W Resistor  
 R8 \_\_\_\_\_ 33K 1/4W Resistor  
 R9 \_\_\_\_\_ 150K 1/4W Resistor  
 R10 \_\_\_\_\_ 500R 1/2W Trimmer Cermet  
 R11 \_\_\_\_\_ 39R 1/4W Resistor  
 R14,R15 \_\_\_\_\_ R33 2.5W Resistors  
 R16 \_\_\_\_\_ 10R 2.5W Resistor  
 R17 \_\_\_\_\_ R22 5W Resistor (wirewound)

C1 \_\_\_\_\_ 470nF 63V Polyester Capacitor  
 C2 \_\_\_\_\_ 470pF 63V Polystyrene or ceramic Capacitor  
 C3 \_\_\_\_\_ 47μF 63V Electrolytic Capacitor  
 C4,C8,C9,C11 \_\_\_\_ 100nF 63V Polyester Capacitors  
 C5 \_\_\_\_\_ 10pF 63V Polystyrene or ceramic Capacitor  
 C6 \_\_\_\_\_ 1μF 63V Polyester Capacitor  
 C7,C10 \_\_\_\_\_ 100μF 63V Electrolytic Capacitors

D1,D2,D3 \_\_\_\_ 1N4002 100V 1A Diodes



## Comments:

To celebrate the hundredth design posted to this website, and to fulfil the requests of many correspondents wanting an amplifier more powerful than the 25W MosFet, a 60 - 90W High Quality power amplifier design is presented here.

Circuit topology is about the same of the above mentioned amplifier, but the extremely rugged IRFP240 and IRFP9240 MosFet devices are used as the output pair, and well renowned high voltage Motorola's transistors are employed in the preceding stages.

The supply rails voltage was kept prudentially at the rather low value of + and - 40V. For those wishing to experiment, the supply rails voltage could be raised to + and - 50V maximum, allowing the amplifier to approach the 100W into 8 Ohm target: enjoy!

A matching, discrete components, Modular Preamplifier design is available here: Modular Audio Preamplifier.

## Notes:

A small, U-shaped heatsink must be fitted to Q6 & Q7.

Q8 & Q9 must be mounted on large heatsinks.

Quiescent current can be measured by means of an Avo-meter wired in series to the positive supply rail and no input signal.

Set the Trimmer R10 to its minimum resistance.

Power-on the amplifier and adjust R10 to read a current drawing of about 120 - 130mA.

Wait about 15 minutes, watch if the current is varying and readjust if necessary.

The value suggested for C1 and C2 in the Power Supply Parts List is the minimum required for a mono amplifier. For optimum performance and in stereo configurations, this value should be increased: 10000µF is a good compromise.

A correct grounding is very important to eliminate hum and ground loops. Connect to the same point the ground sides of R1, R3, C2, C3 and C4 and the ground input wire. Connect R7 and C7 to C11 to output ground. Then connect separately the input and output grounds to the power supply ground.

---

## Technical data:

Output power: 60 Watt RMS @ 8 Ohm (1KHz sinewave) - 90W RMS @ 4 Ohm

Sensitivity: 1V RMS input for 58W output

Frequency response: 30Hz to 20KHz - 1dB

Total harmonic distortion @ 1KHz: 1W 0.003% 10W 0.006% 20W 0.01% 40W 0.013% 60W 0.018%

Total harmonic distortion @10KHz: 1W 0.005% 10W 0.02% 20W 0.03% 40W 0.06% 60W 0.09%

Unconditionally stable on capacitive loads