
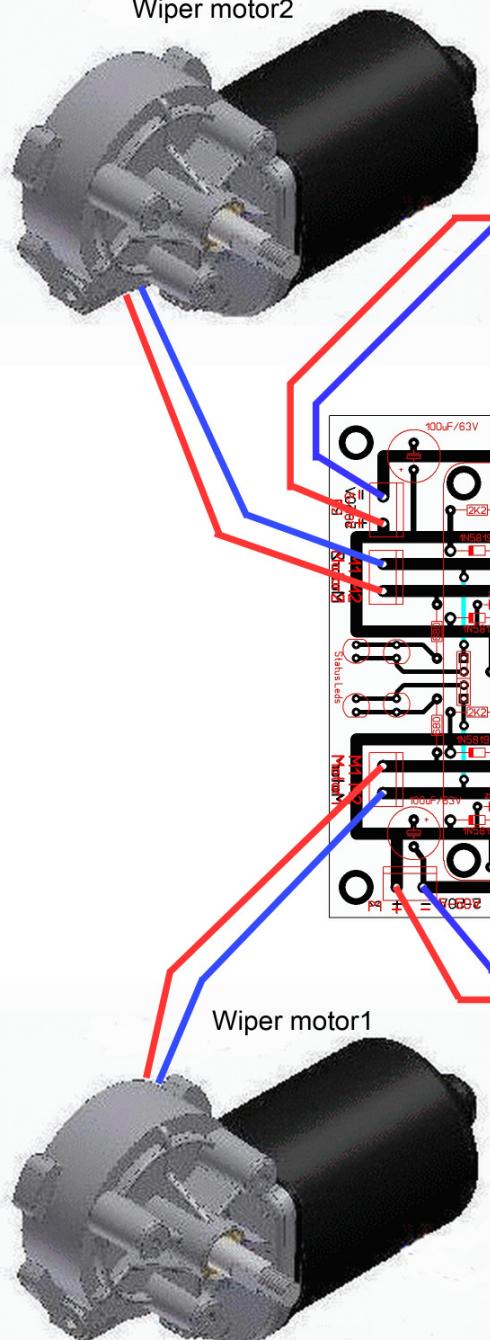



Wiper motor2

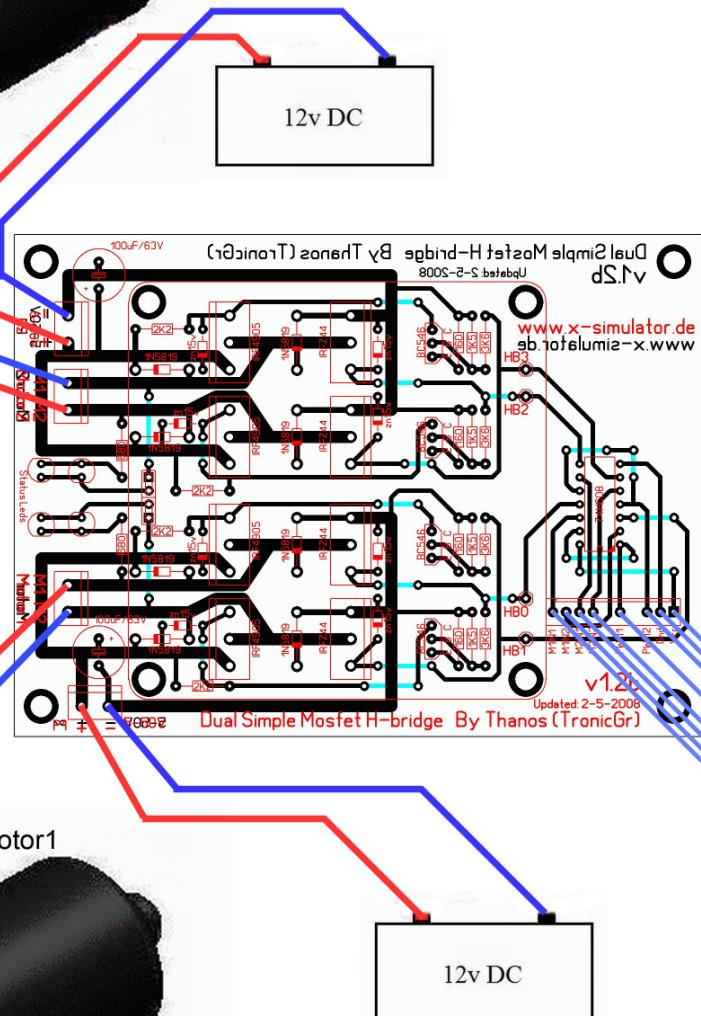


Connection Diagram of the AMC1.5 and DSMhb1.2b with two wiper motors and two potentiometers




Potentiometer1 for motor1

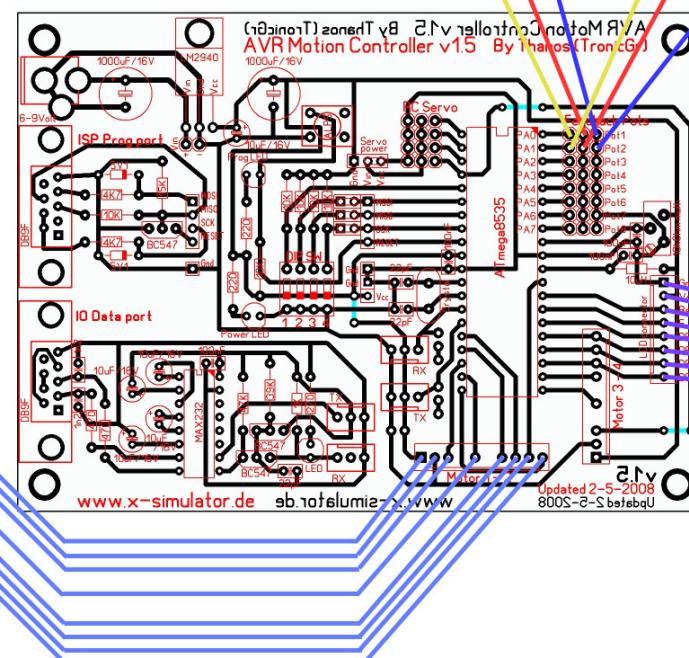

Potentiometer2 for motor2

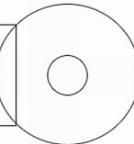

Parallel LCD module

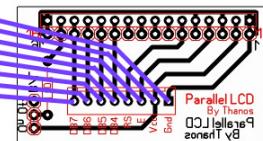

By Thanos (TronicGr) Greece 2008